
Civil Drawing – Plan and Elevation


Plan

```
Civil drawing
    Plan
    Elevation
    Walls, Beams, Columns, Doors, Windows etc..
    Scaling
Electrical Drawing
    Basic Symbols
    3-phase and 1-phase wiring diagrams
    Substation layout
```


Block Diagram

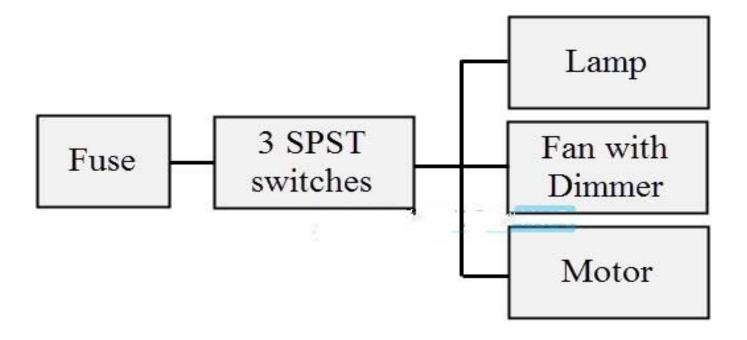

Schematic Diagram

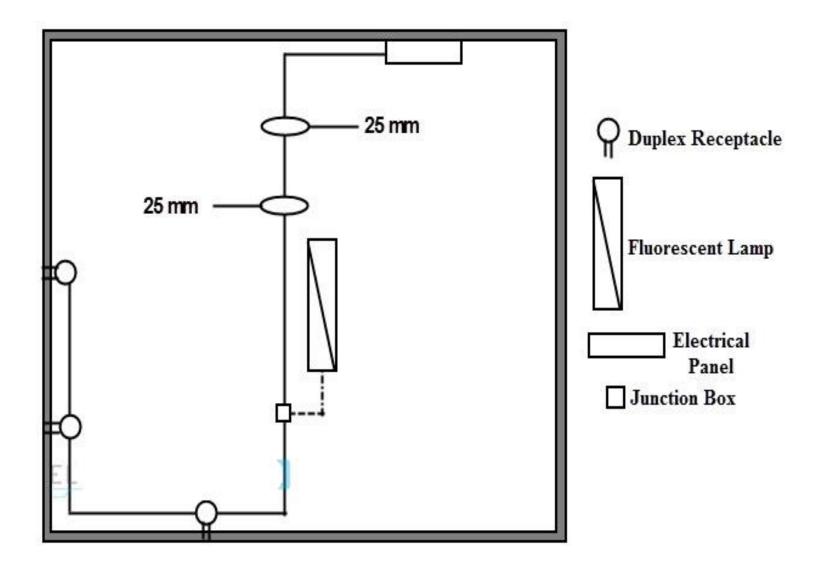

Wiring Diagram

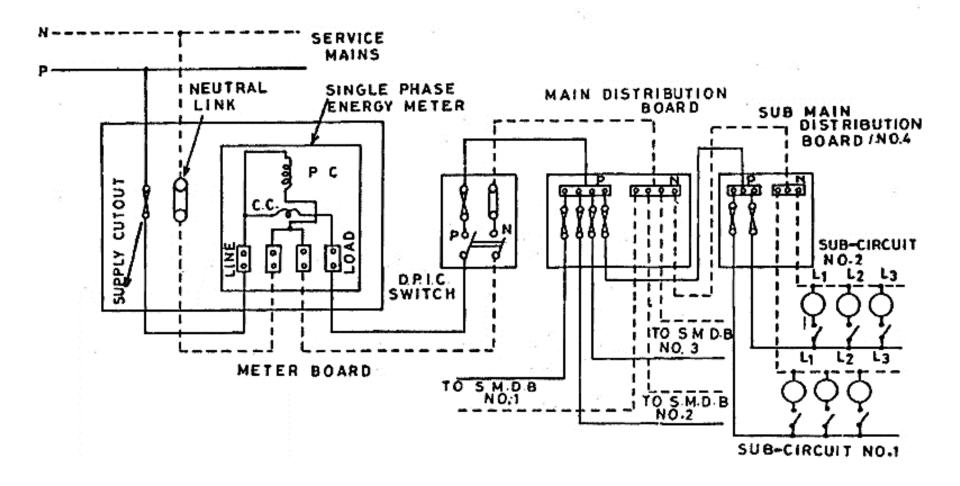

Quiz

- Draw a schematic diagram for two rooms having 2 LEDs, 1 ceiling fan, 1 circuit board (switch board) and 1 split each. These rooms are connected to a sub main distribution board then to a main switch then to a 3-phase main distribution board.
- Draw a wiring diagram for two rooms having 2 LEDs, 1 ceiling fan, 1 circuit board (switch board) and 1 split each. These rooms are connected to a sub main distribution board then to a main switch then to a 3-phase main distribution board.